

# VLSI Design Tutorial - NGSPICE

Abhishek Srivastava

Assistant Professor

CVEST, IIIT Hyderabad



INTERNATIONAL INSTITUTE OF  
INFORMATION TECHNOLOGY

---

H Y D E R A B A D

# About NGSPICE, download and install

- SPICE : Simulation Program with Integrated Circuit Emphasis
- NGSPICE is an open source mixed-signal circuit simulator which can be used to perform different analysis on a circuit
- For SPICE, any circuit is described as an interconnection of various active, passive elements. This interconnection of elements is also called **Net-List**
- Parameters to capture physical behaviour of active devices can be included as **Model File**. For example BSIM1 to BSIM6 are SPICE models for various types of transistors developed by UC Berkley (Berkeley Short-channel IGFET Model)
- DC, transient, AC, pole-zero, noise, PSS - analysis can be performed using NGSPICE
- Result plots can be viewed and saved
- Download NGSPICE from following path and install:  
*<http://ngspice.sourceforge.net/download.html>*
- NGSPICE manual can be also downloaded from the same site

# General structure of a Net-List

- Circuit description
- Models used to describe circuit elements may be included
- Type of analysis to be done on the circuit
- Control commands to run the simulation and plot/save the results

*Note: Commands in NGSPICE are case insensitive*

# Example to illustrate NGSPICE usage

## *Net list of simple RC circuit*

Simple RC low pass configuration

\* First line is the title. '\*' used for comments

\* Circuit discription

R1 in out 1k

C2 out 0 1nf

\* input pulse

vin in 0 pulse 0 5 0ns 100ns 100ns 10us 20us

\* Type of analysis is transient

.tran 10n 60u

.control



run

plot v(in) v(out)

\* Saving plots to ps file

hardcopy rc\_ckt\_tr\_out\_1.eps v(in) v(out)

.endc

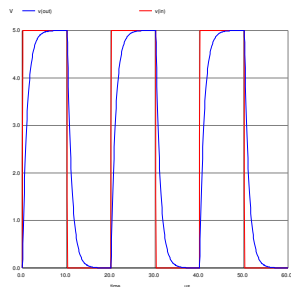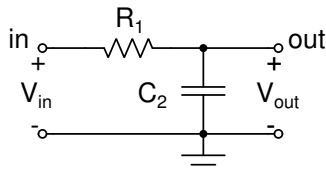

# Example to illustrate DC analysis

## MOS $I_{DS}$ - $V_{GS}$ curve

Netlist to evaluate MOS  $I_D$ - $V_{GS}$  characteristics

```
.include TSMC_180nm.txt
.param SUPPLY=1.8
.param LAMBDA=0.09u
.param width_N={20*LAMBDA}
.global gnd vdd
VGS G gnd 'SUPPLY'
VDS D gnd 1V
M1 D G gnd gnd CMOSN W={width_N} L={2*LAMBDA} +
AS={5*width_N*LAMBDA} PS={10*LAMBDA+2*width_N}
AD={5*width_N*LAMBDA}
PD={10*LAMBDA+2*width_N}
.dc VGS 0 1.8 0.05
.control
run
plot -VDS#branch
set hcopypscolor = 1 *White background
hardcopy mos_id_vg.eps -VDS#branch
.endc
```

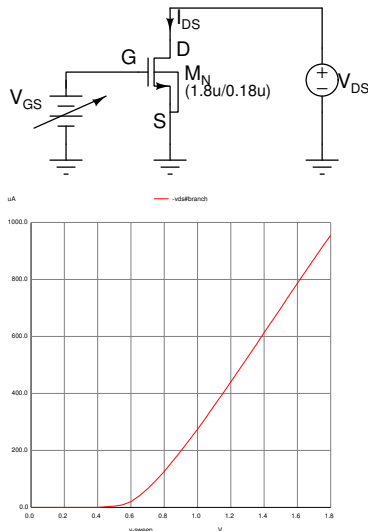


Figure:  $I_{DS}$  Vs  $V_{GS}$

# Example to illustrate Transient analysis

## CMOS Inverter transient analysis

CMOS inverter transient response

```
.include TSMC_180nm.txt
```

```
.param SUPPLY=1.8
```

```
.param LAMBDA=0.09u
```

```
.param width_P=20*LAMBDA
```

```
.param width_N=10*LAMBDA
```

```
.global gnd vdd
```

```
Vdd vdd gnd 'SUPPLY'
```

```
vin x gnd pulse 0 1.8 0ns 1ns 1ns 10ns 20ns
```

```
M1 y x gnd gnd CMOSN W={width_N} L={2*LAMBDA} +  
AS={5*width_N*LAMBDA} PS={10*LAMBDA+2*width_N}  
AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}
```

```
M2 y x vdd vdd CMOSP W={width_P} L={2*LAMBDA} +  
AS={5*width_P*LAMBDA} PS={10*LAMBDA+2*width_P}  
AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}
```

```
Cout y gnd 100f
```

```
.tran 0.1n 200n .control
```

```
run
```

```
plot v(y) v(x)
```

```
set hcopyscolor = 1
```

```
hardcopy inv_transient_resp.eps v(x) v(y)
```

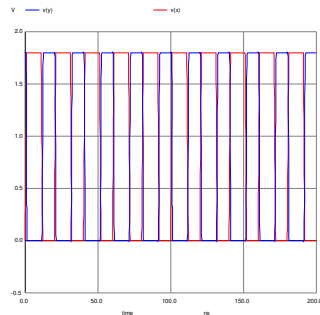
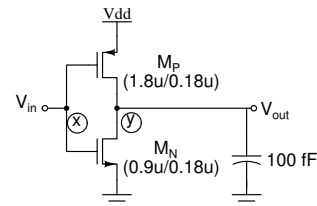


Figure: Transient response of CMOS Inverter

# Example to illustrate .SUBCKT usage

## *Describing CMOS inverter using subckt*

CMOS inverter transient response

```
.include TSMC_180nm.txt
.param SUPPLY=1.8
.param LAMBDA=0.09u
.global gnd vdd

Vdd vdd gnd 'SUPPLY'
vin a gnd pulse 0 1.8 0ns 1ns 1ns 10ns 20ns

.subckt inv y x vdd gnd width_P=20*LAMBDA
width_N=10*LAMBDA
.param width_P=20*LAMBDA
.param width_N=10*LAMBDA

M1 y x gnd gnd CMOSN W={width_N} L={2*LAMBDA} +
AS={5*width_N*LAMBDA} PS={10*LAMBDA+2*width_N}
AD={5*width_N*LAMBDA} PD={10*LAMBDA+2*width_N}

M2 y x vdd vdd CMOSP W={width_P} L={2*LAMBDA} +
AS={5*width_P*LAMBDA} PS={10*LAMBDA+2*width_P}
AD={5*width_P*LAMBDA} PD={10*LAMBDA+2*width_P}

.ends inv

x1 b a vdd gnd inv width_P=20*LAMBDA width_N=10*LAMBDA
Cout b gnd 100f

.tran 0.1n 200n .control
run
plot v(b) v(a)
set hcopypscolor = 1
hardcopy inv_transient_resp_subckt.eps v(b) v(a)
```

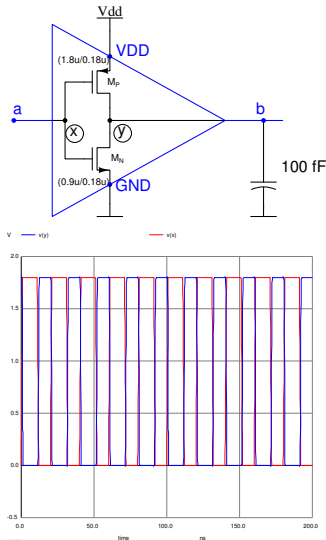


Figure: Transient response of CMOS Inverter

# Quick keys I

- To launch NGSPICE  
*ngspice* : It will take you to ngspice shell  
*ngspice file\_name.<cir or sp>* : It will execute the specified net-list
- Type quit or exit to end the ngspice shell
- To execute a net-list in ngspice shell  
*ngspice —> source filename*
- To edit in ngspice shell  
*ngspice —> edit file\_name ; :wq!* to save and quit editing
- To run an analysis specified in net-list in ngspice shell  
*ngspice —> run*
- To plot in ngspice shell  
use 'plot' command



# Quick keys II

- To plot voltages

*ngspice*  $\rightarrow$  *plot v(node\_name)*

Ex. plot v(out) v(in)

- To plot branch currents

*plot voltage\_source\_name#btranch*

Ex. plot VDS#branch

– Note that direction of current is entering into the positive terminal of a voltage source

– If required a dummy 0 V DC source can be inserted in the net-list to plot branch current

- To save plots as ps

*hardcopy file\_name.eps variables\_to\_plot*

Ex. hardcopy inv\_transient\_resp.eps v(x) v(y)

- To change background colour of saved plot

set hcopypscolor = 1 \*White background

## Quick keys III

- To change background colour plot window  
set color0=white \*\* color0 is used to set the background of the plot (manual sec:17.7)  
set color1=black \*\* color1 is used to set the grid color of the plot (manual sec:17.7)
- Specifying pulse  
vin in+ in- pulse  $V_{Low}$   $V_{High}$  delay rise-time fall-time on-period time-period  
vin in 0 pulse 0 5 0ns 100ns 100ns 10us 20us
- Specifying sinusoidal signal  
SIN(VO VA FREQ TD THETA PHASE)  
Ex. vin a 0 sin(.849 0.25 50Meg 0 0)
- DC analysis  
.dc *voltage\_to\_be\_swept*  $V_{initial}$   $V_{final}$  *step\_size*  
Ex: .dc vgs 0v 1.8v 0.1

# Quick keys IV

- Transient analysis

`.tran step_size stop_time < start_time >`

Ex: `.tran 10n 60u`

- AC analysis

`.ac lin number_of_points start stop`

`.ac lin 100 1 100Hz`

- Measure statement example (sec 15.4.5):

`.measure tran tpdf`

+ TRIG v(1) VAL='SUPPLY/2' RISE=1

+ TARG v(2) VAL='SUPPLY/2' Fall=1

measures the time difference between v(1) reaching 'SUPPLY/2' V for the first time on its first rising slope (TRIG) versus v(2) reaching 'SUPPLY/2' V for the first time on its first falling slope (TARG), i.e. it measures the fall time delay between v(1) and v(2).

- Refer NGSPICE manual for more details